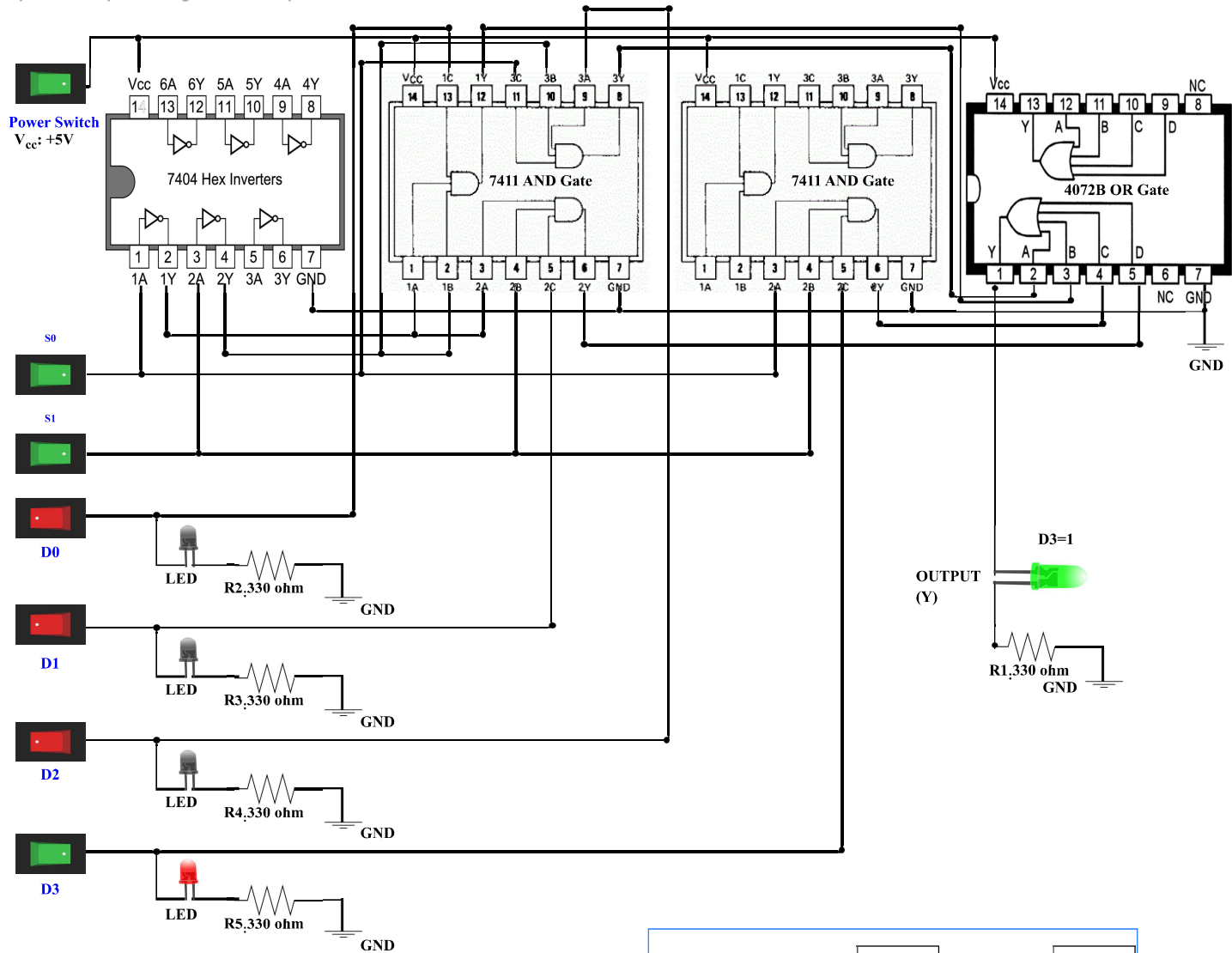


INSTRUCTIONS

Experiment to perform logic of 4:1 Multiplexer on kit



TRUTH TABLE		PRINT	Add	
Serial No.	S0	S1	OUTPUT (Y)	OUTPUT VALUE
1	0	0	D0	1
2	0	1	D1	1
3	1	0	D2	1
4	1	1	D3	1